

# A practical approach to detect turn to turn shorts during superconductive magnet fabrication

Giovanni Gabrielli

Supervisor: Luciano Elementi

Coordinator: Emanuela Barzi

Fermilab National Accelerator Laboratory


September 27, 2013




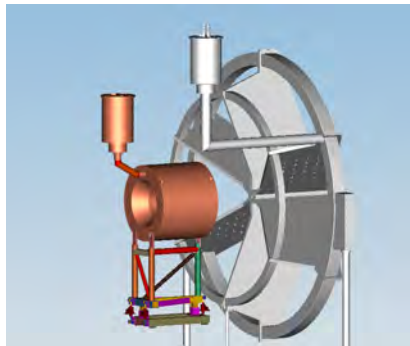
# CLAS12 for Hall B experiment

Six superconductive coils, forming a toroidal magnet, generate a toroidal magnetic field in order to deviate the debris coming from collisions between particles.

Each magnet is a double layered  $Nb_3Sn$  coil with 117 turns per layer, wound, clamped and cured in Technical Division.



# Turn to turn shorts

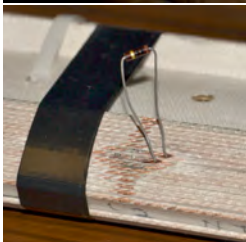
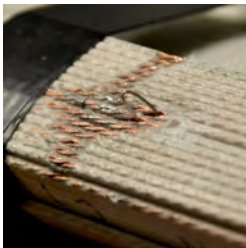


What is a short?

- It is an electrical contact between two consecutive turns



# Turn to turn shorts

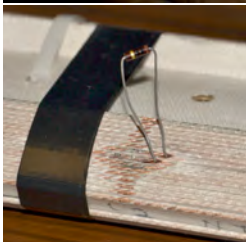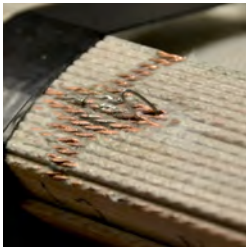


What is a short?

- It is an electrical contact between two consecutive turns
- It may appear at any time, most probably during winding or clamping



# Turn to turn shorts

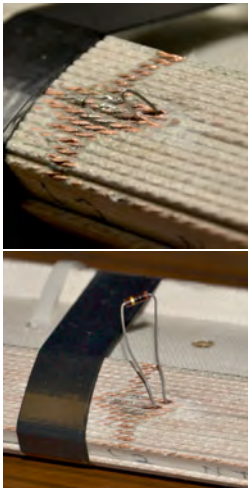


What is a short?

- It is an electrical contact between two consecutive turns
- It may appear at any time, most probably during winding or clamping
- Its model is a small resistance  $R$ , inversely proportional to the area and the pressure of the contact between the turns



# Turn to turn shorts

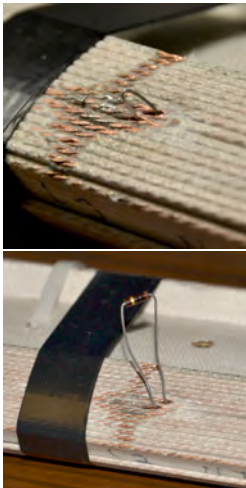


What is a short?

- It is an electrical contact between two consecutive turns
- It may appear at any time, most probably during winding or clamping
- Its model is a small resistance  $R$ , inversely proportional to the area and the pressure of the contact between the turns
- Hard shorts are  $\approx 0 \Omega$ , soft shorts can be several  $\Omega$



# Turn to turn shorts

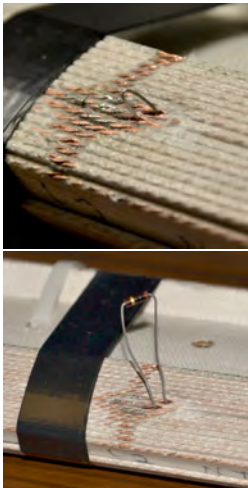

What is a short?

- It is an electrical contact between two consecutive turns
- It may appear at any time, most probably during winding or clamping
- Its model is a small resistance  $R$ , inversely proportional to the area and the pressure of the contact between the turns
- Hard shorts are  $\approx 0 \Omega$ , soft shorts can be several  $\Omega$
- Simulated with resistors or wires (see pictures)



# CLAS12 turn to turn short detector

## Task

Detect turn to turn shorts, both hard and as soft as possible.

Problems:

Solution:





# CLAS12 turn to turn short detector

## Task

Detect turn to turn shorts, both hard and as soft as possible.

Problems:

- Novel approach

Solution:



# CLAS12 turn to turn short detector

## Task

Detect turn to turn shorts, both hard and as soft as possible.

Problems:

- Novel approach
- TL theory doesn't work

Solution:



# CLAS12 turn to turn short detector

## Task

Detect turn to turn shorts, both hard and as soft as possible.

### Problems:

- Novel approach
- TL theory doesn't work
- Very low DC resistance

### Solution:



# CLAS12 turn to turn short detector

## Task

Detect turn to turn shorts, both hard and as soft as possible.

### Problems:

- Novel approach
- TL theory doesn't work
- Very low DC resistance

### Solution:

- AC steady state, high frequency, high impedance



# CLAS12 turn to turn short detector

## Task

Detect turn to turn shorts, both hard and as soft as possible.

### Problems:

- Novel approach
- TL theory doesn't work
- Very low DC resistance

### Solution:


- AC steady state, high frequency, high impedance
- Significant voltage drop between turns



# AC impedance analysis

## Setup:

- Inductive zone:  
 $|Z| \approx \omega L$ , rising with frequency

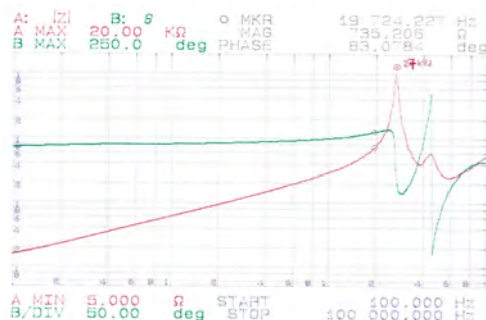


**Figure:** Double layered unclamped coil AC impedance



# AC impedance analysis

## Setup:

- Inductive zone:  
 $|Z| \approx \omega L$ , rising with frequency
- Each turn has higher impedance

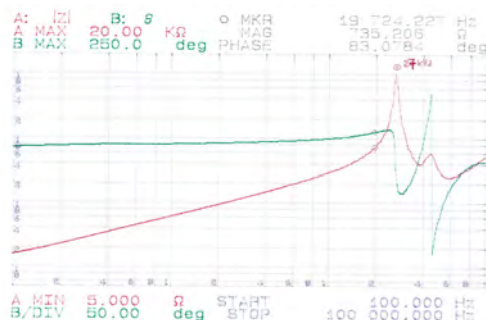


**Figure:** Double layered unclamped coil AC impedance



# AC impedance analysis

## Setup:

- Inductive zone:  
 $|Z| \approx \omega L$ , rising with frequency
- Each turn has higher impedance
- Softer short are more easily detectable

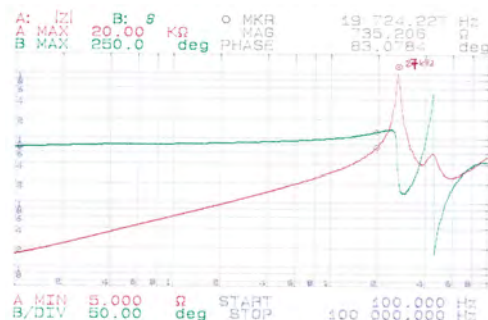

**Figure:** Double layered unclamped coil AC impedance






# AC impedance analysis

## Setup:

- Inductive zone:  
 $|Z| \approx \omega L$ , rising with frequency
- Each turn has higher impedance
- Softer short are more easily detectable
- High frequency needed

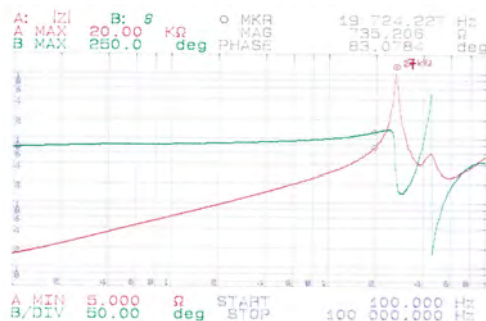


**Figure:** Double layered unclamped coil AC impedance

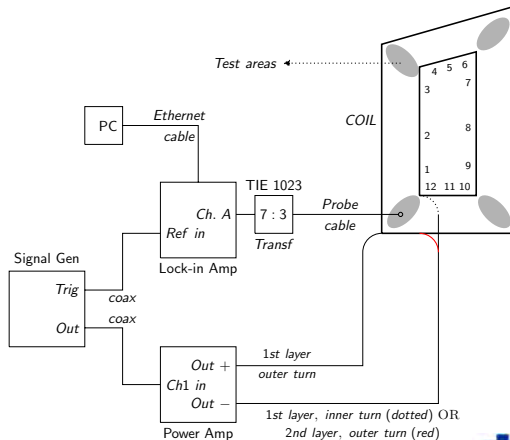

# General setup


Setup:



# General setup

Setup:


- 19.8 kHz sine wave

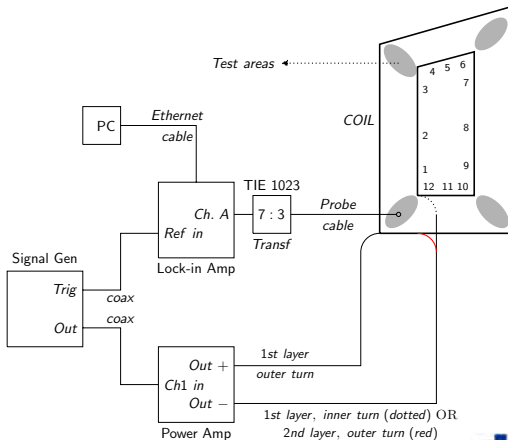

# General setup

## Setup:

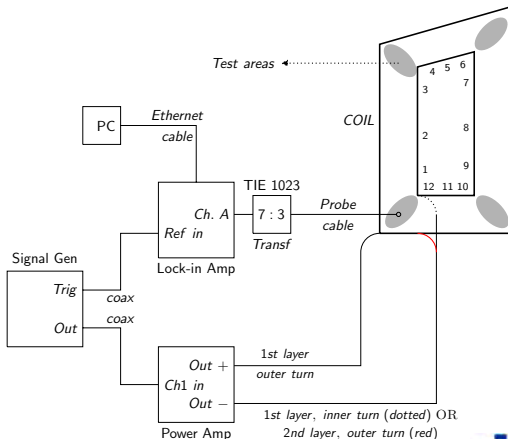
- 19.8 *kHz* sine wave
- 30  $V_{RMS}$  output



# General setup

## Setup:

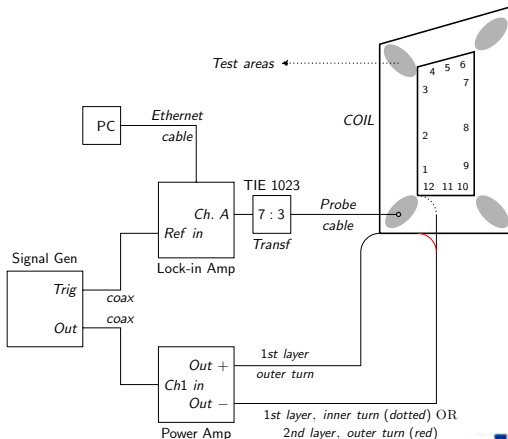
- 19.8 *kHz* sine wave
- 30  $V_{RMS}$  output
- 3:7 step-up transformer



# General setup

## Setup:

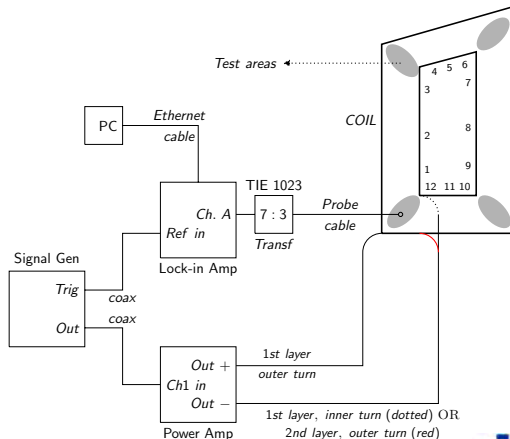- 19.8 *kHz* sine wave
- 30  $V_{RMS}$  output
- 3:7 step-up transformer
- Automatic data acquisition:  
LabView driver



# Transformer

Transformer:

- Required by the Lock-in Amplifier



# Transformer

Transformer:

- Required by the Lock-in Amplifier
- Low CMRR, huge offset





# Transformer

Transformer:

- Required by the Lock-in Amplifier
- Low CMRR, huge offset
- "Walking effect"



# Transformer

Transformer:

- Required by the Lock-in Amplifier
- Low CMRR, huge offset
- "Walking effect"
- Parasitic asymmetric capacitive coupling




# Transformer

## Transformer:

- Required by the Lock-in Amplifier
- Low CMRR, huge offset
- "Walking effect"
- Parasitic asymmetric capacitive coupling
- Handmade transformer: more distant coils, high frequency wire, negligible parasitic effects




# LabView Driver

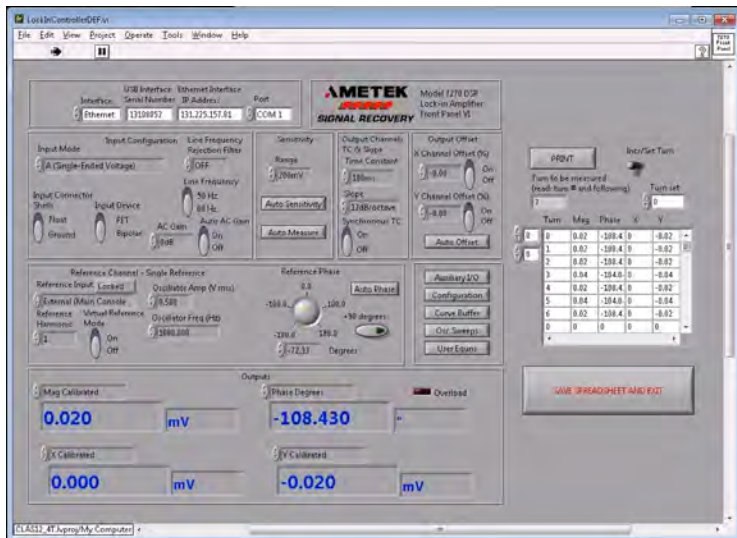

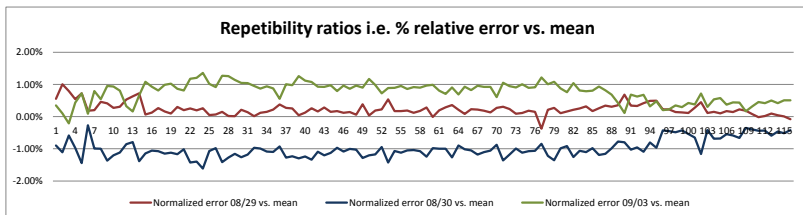
# Procedure

- 1 A few scanings of all turns, one position (corner 1-12), to see repeatability, that is the precision of the method



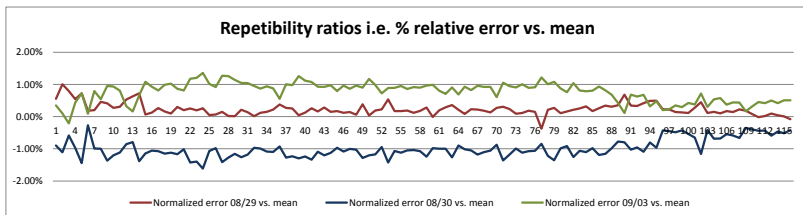
# Procedure


- 1 A few scannings of all turns, one position (corner 1-12), to see repeatability, that is the precision of the method
- 2 Scannings with different shorts to see position and amount of turn to turn voltage losses, that is the sensitivity and resolution of the method.



# Non shorted coil voltage curve

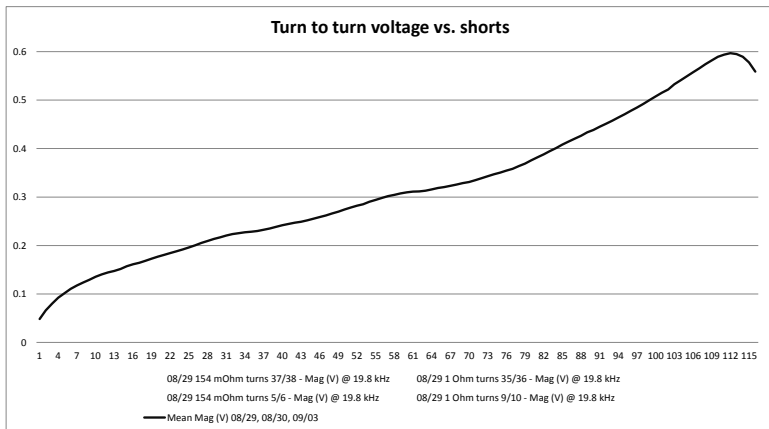

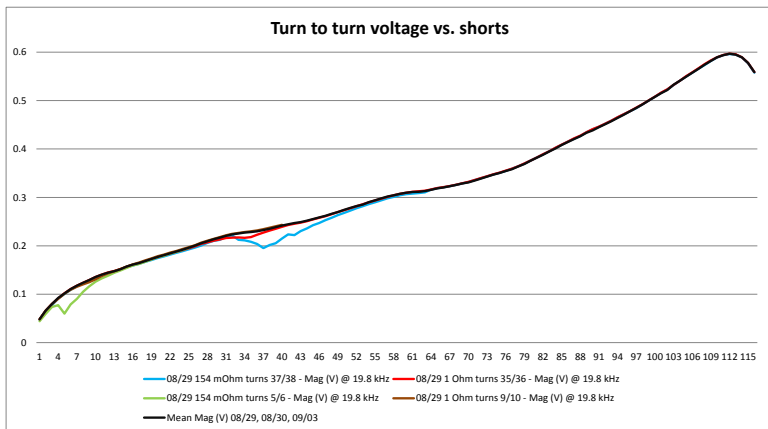
# Non shorted vs. shorted coil voltage curves






# Voltage losses


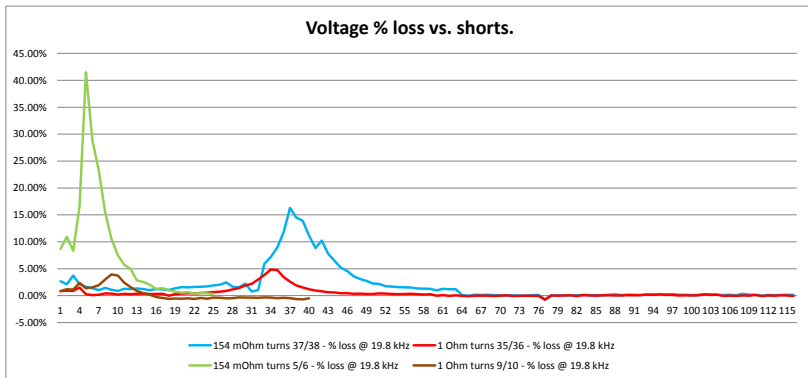

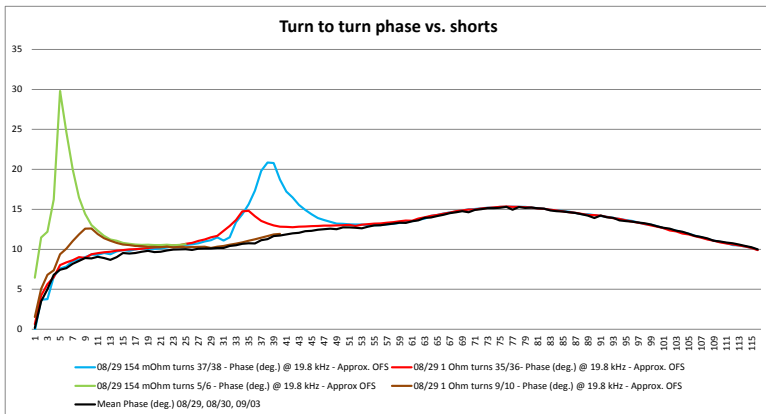
# Non shorted vs. shorted coil phase curves


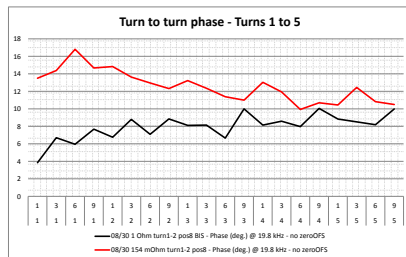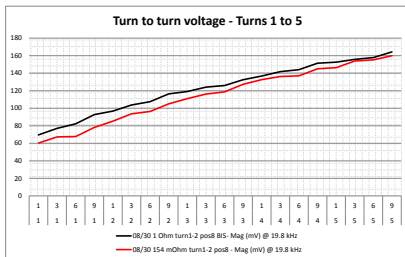
# 4 position method

In the very first turns it is harder to see a sharp loss with a smooth bending by its sides. A 4-position scanning can help increase the resolution.



NB: with low SNR, the help of the phase is fundamental.



# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example



# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example

- $|Z_{coil}| = 735\ \Omega$



# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example

- $|Z_{coil}| = 735\ \Omega$
- $|Z_{turn}| \approx \frac{|Z_{coil}|}{117.2} \approx 3\ \Omega$



# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example

- $|Z_{coil}| = 735\ \Omega$
- $|Z_{turn}| \approx \frac{|Z_{coil}|}{117.2} \approx 3\ \Omega$
- $|Z_{short}| = 150\ m\Omega$



# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example

- $|Z_{coil}| = 735\ \Omega$
- $|Z_{turn}| \approx \frac{|Z_{coil}|}{117.2} \approx 3\ \Omega$
- $|Z_{short}| = 150\ m\Omega$
- $Loss \approx 1 - \frac{|Z_{short}|}{|Z_{turn}|} \approx 95\%$





# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example

- $|Z_{coil}| = 735\ \Omega$
- $|Z_{turn}| \approx \frac{|Z_{coil}|}{117.2} \approx 3\ \Omega$
- $|Z_{short}| = 150\ m\Omega$
- $Loss \approx 1 - \frac{|Z_{short}|}{|Z_{turn}|} \approx 95\%$

## Problems

- 1 Why don't we ever see such huge losses?



# Conclusions and problems

Resolution: up to  $1\ \Omega$  in middle turns, up to a few hundreds  $m\Omega$  in the first 5. But:

## Example

- $|Z_{coil}| = 735\ \Omega$
- $|Z_{turn}| \approx \frac{|Z_{coil}|}{117.2} \approx 3\ \Omega$
- $|Z_{short}| = 150\ m\Omega$
- $Loss \approx 1 - \frac{|Z_{short}|}{|Z_{turn}|} \approx 95\%$


## Problems

- 1 Why don't we ever see such huge losses?
- 2 Why should a short influence even the nearest turns?




# Zero model for currents in a shorted coil

- Shorted turn (in red) is "bypassed"

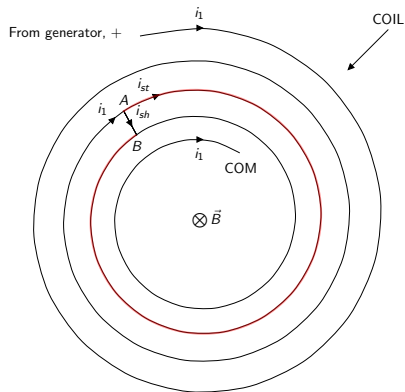


# Zero model for currents in a shorted coil

- Shorted turn (in red) is "bypassed"
- $B \propto V$  const,  $i_1 \propto \frac{1}{|Z_{coil}|}$  rises slightly

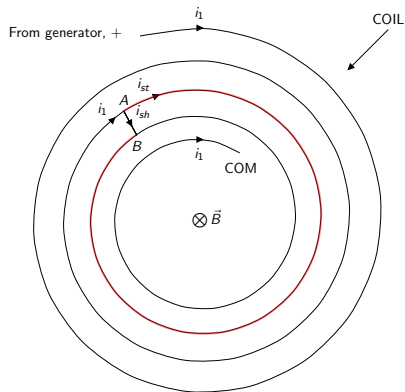


# Zero model for currents in a shorted coil

- Shorted turn (in red) is "bypassed"
- $B \propto V$  const,  $i_1 \propto \frac{1}{|Z_{coil}|}$  rises slightly
- High  $i_{st} < 0$  generates high  $B_{st} < 0$  to compensate  $B_{tot}$

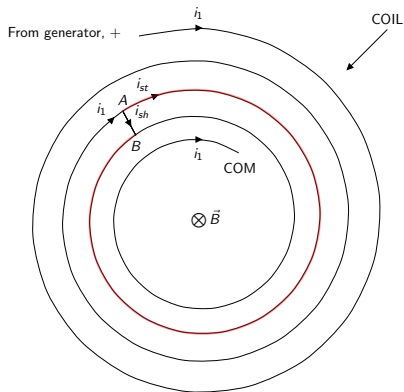


# Zero model for currents in a shorted coil

- Shorted turn (in red) is "bypassed"
- $B \propto V$  const,  $i_1 \propto \frac{1}{|Z_{coil}|}$  rises slightly
- High  $i_{st} < 0$  generates high  $B_{st} < 0$  to compensate  $B_{tot}$
- High  $i_{sh}$  gives relatively high voltage drop  $V_{sh}$

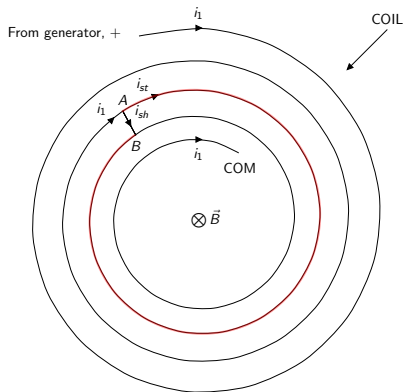


Zero model for currents in a shorted coil

# What (almost) really happens

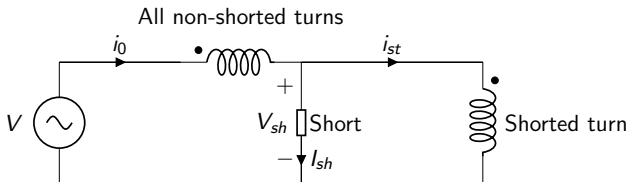

Zero model for currents in a shorted coil

# What (almost) really happens

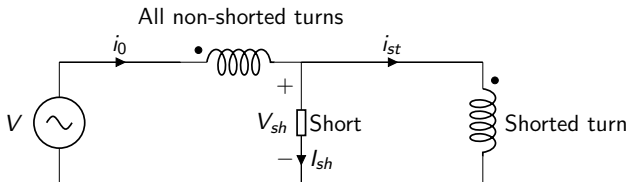


- Mutual induction: the shorted turn is the "secondary"





Zero model for currents in a shorted coil

# What (almost) really happens

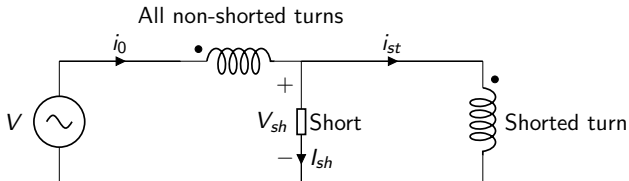


- Mutual induction: the shorted turn is the "secondary"
- $V_{st}$  is still positive because of Lenz's Law



Zero model for currents in a shorted coil


# What (almost) really happens

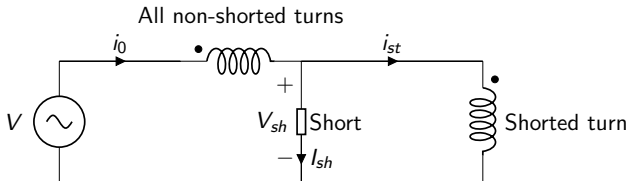

- Mutual induction: the shorted turn is the "secondary"
- $V_{st}$  is still positive because of Lenz's Law
- $B_{st} < 0$  influences mostly the nearest turns



# What (almost) really happens

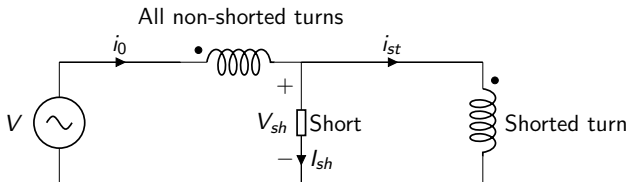

- Mutual induction: the shorted turn is the "secondary"
- $V_{st}$  is still positive because of Lenz's Law
- $B_{st} < 0$  influences mostly the nearest turns

Despite this is a zero model, experimental data fit this theoretical result with good approximation.



# High Resolution DC resistance measure

## Task

Measure small DC resistances with as high precision as possible.



# High Resolution DC resistance measure

## Task

Measure small DC resistances with as high precision as possible.

- 4-wire measurement with  $8\frac{1}{2}$  digits resolution multimeter 3458A from Agilent: less than 4 significant digits for a  $1\ \Omega$  shunt.



# High Resolution DC resistance measure

## Task


Measure small DC resistances with as high precision as possible.

- 4-wire measurement with  $8\frac{1}{2}$  digits resolution multimeter 3458A from Agilent: less than 4 significant digits for a  $1\ \Omega$  shunt.
- "Enhanced 4W" needed: higher currents for very low resistances.



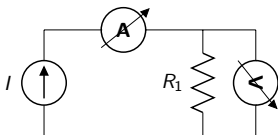
# Measuring the shunts

- ① 3458A as ammeter,  $I \approx 1 \text{ A}$   
imposed, measured  
 $R_1 \approx 1 \Omega$  with 5 significant  
digits.



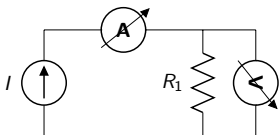
# Measuring the shunts

- ① 3458A as ammeter,  $I \approx 1\text{ A}$  imposed, measured  $R_1 \approx 1\ \Omega$  with 5 significant digits.



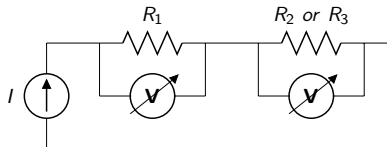
- ② 3458A as voltmeter on  $R_1$  as shunt,  $I \approx 1\text{ A}$  imposed, measured  $R_2 \approx 10\text{ m}\Omega$  and  $R_3 \approx 1\text{ m}\Omega$  with 4 and 3 significant digits.





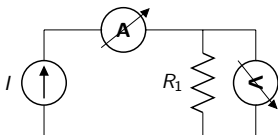
# Measuring the shunts

- ① 3458A as ammeter,  $I \approx 1\text{ A}$  imposed, measured  $R_1 \approx 1\ \Omega$  with 5 significant digits.



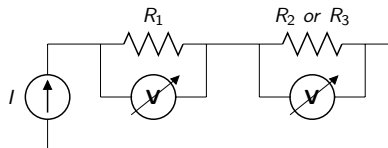- ② 3458A as voltmeter on  $R_1$  as shunt,  $I \approx 1\text{ A}$  imposed, measured  $R_2 \approx 10\text{ m}\Omega$  and  $R_3 \approx 1\text{ m}\Omega$  with 4 and 3 significant digits.




- ③ The same way with just  $R_2$  and  $R_3$  to double check their ratio at higher currents.


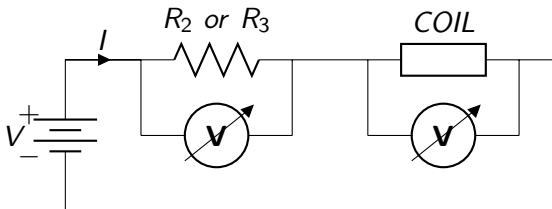
# Measuring the coil

- ④ Coil as load,  $R_2$  and  $R_3$  as shunts, currents from 1 to 10 A.  
Measured  $R_{coil}$  with no less than 3 significant digits.  
NB: Voltage source used because current source did not work with reactive loads.



# Shunts

Im avg	Va avg	Vb avg	Vc avg	Ra avg	Rb avg	Rc avg
1.00538	1.00577	10.02065	0.9955	<b>1.000387913</b>	<b>9.967027393</b>	<b>0.99017287</b>
0.901365	0.90175	8.9885	0.8928	1.00042713	9.972097874	0.990497745
0.8944	0.89479	8.909	0.885	1.000436047	9.960867621	0.989490161
0.89587		8.9345	0.8884		9.972987152	0.991661737
Average:				<b>1.00041703</b>	<b>9.967839188</b>	<b>0.99066020</b>
St. Dev.				<b>0.00002091</b>	<b>0.003986671</b>	<b>0.00074192</b>
% St. Dev.				<b>0.002090%</b>	<b>0.039995%</b>	<b>0.074891%</b>
Final values:				<b>1.0004</b>	<b>9.968</b>	<b>0.991</b>



# Small test coil

Vshunt (mV)	Rshunt (mOhms)	I meas (A)	Vcoil (mV)	R coil (mOhms)
10.325	9.968	1.035814607	26.919	25.98824136
20.831	9.968	2.089787319	54.315	25.99068312
40.791	9.968	4.092195024	106.33	25.98361011
70.705	9.968	7.093198234	184.3	25.98263772
102.76	9.968	10.30898876	267.95	25.99188011
1.025	0.991	1.034308779	26.876	25.98450341
2.0755	0.991	2.094349142	54.397	25.97322428
4.062	0.991	4.09889001	106.46	25.97288528
7.045	0.991	7.108980827	184.65	25.97418737
10.224	0.991	10.31685166	268.1	25.98660994

**Average:** 25.98284627

**St. Dev.** 0.00675612

**% St.Dev.** 0.0260%

**R:** 25.98

4 significant digits.



## CLAS12 coil

Vshunt (mV)	Rshunt (mOhms)	I meas (A)	Vcoil (V)	R coil (mOhms)
10.767	9.968	1.080156501	0.9124	844.692412
26.497	9.968	2.65820626	2.2447	844.4416198
65.198	9.968	6.540730337	5.5207	844.0494739
102.34	9.968	10.26685393	8.664	843.8807114
1.113	0.991	1.123107972	0.9484	844.4424079
2.589	0.991	2.612512614	2.205	844.0150637
6.211	0.991	6.26740666	5.2891	843.9056674
10.355	0.991	10.44904137	8.8176	843.8668856

Average: **844.1617802**St. Dev. **0.2967168**% St.Dev. **0.0351%****R:** **844**

3 significant digits, but St. Dev is much less than half of the last digit.



# A practical approach to detect turn to turn shorts during superconductive magnet fabrication

Giovanni Gabrielli

Supervisor: Luciano Elementi

Coordinator: Emanuela Barzi

Fermilab National Accelerator Laboratory

September 27, 2013

